



## Homework 04

Ren-Der Chen (陳仁德)  
Department of Computer Science and  
Information Engineering  
National Changhua University of Education  
E-mail: rdchen@cc.ncue.edu.tw  
Fall, 2019

### Sequence Detector

---

- n A **sequence detector** accepts a string of bits (either 0 or 1) as input.
- n Its output goes to 1 whenever a **target sequence** is detected.
- n There are two types of detection: **overlapping** and **non-overlapping**.
- n For a detector that allows overlapping, the final bits of one sequence can be the start of another sequence.
- n **Overlapping** type will be adopted here.

## Example


---

- n Target sequence: 1011
- n Input sequence: 1 1 0 1 1 0 1 1 0
- n Detection output: 0 0 0 0 1 0 0 1 0

3

## Design 1: Mealy Machine



---

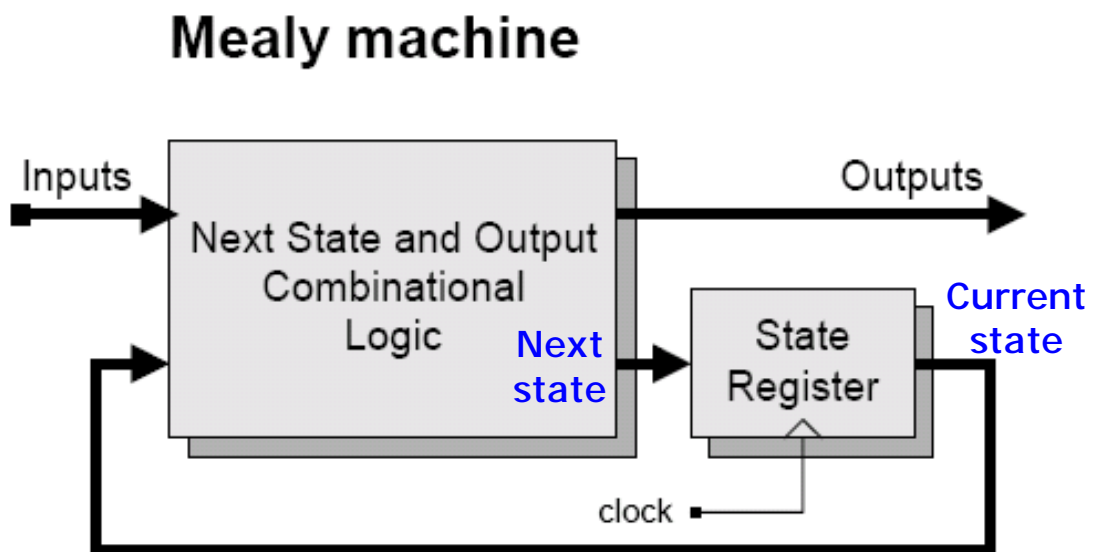

4

# Mealy Machine State Diagram

Target sequence: 1011

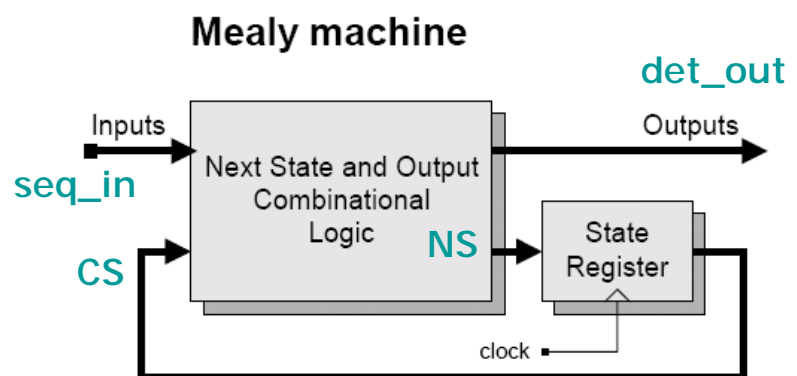 


5

## Verilog Code (1/4)

```
module sd_mealy(clk, rst, seq_in, det_out, state_out);
    input clk, rst, seq_in;
    output reg det_out;
    output [1:0] state_out;
```

```
    parameter
        s0=2'b00,    // no valid seq
        s1=2'b01,    // valid seq: 1
        s2=2'b10,    // valid seq: 10
        s3=2'b11;    // valid seq: 101
```

Four states

 

6

## Verilog Code (2/4)



```

reg [1:0] CS, NS;
// CS: current state
// NS: next state

assign state_out = CS;

// sequential part of the Mealy FSM
always @(posedge clk, posedge rst) begin
    #2
    if (rst==1)
        CS = s0;
    else
        CS = NS;
end

```

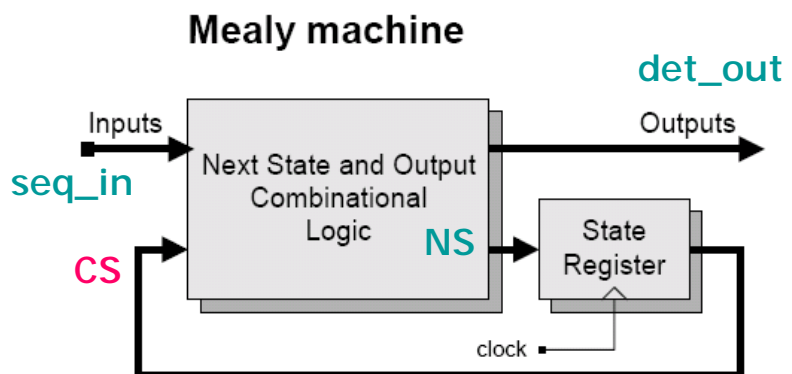 



7

## Verilog Code (3/4)

```

// combinational part of the Mealy FSM
// determine the next state
always @(CS, seq_in) begin
    #2
    case (CS)
        s0: NS = (seq_in==1) ? s1 : s0;
        s1: NS = (seq_in==1) ? s1 : s2;
        s2: NS = (seq_in==1) ? s3 : s0;
        s3: NS = (seq_in==1) ? s1 : s2;
        default: NS = s0;
    endcase
end



```

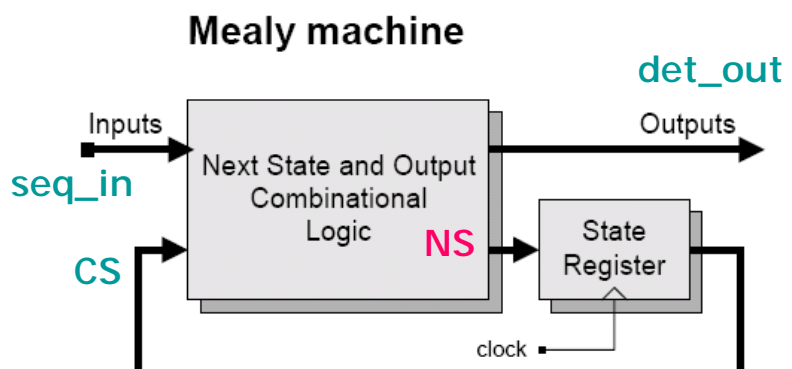 

8

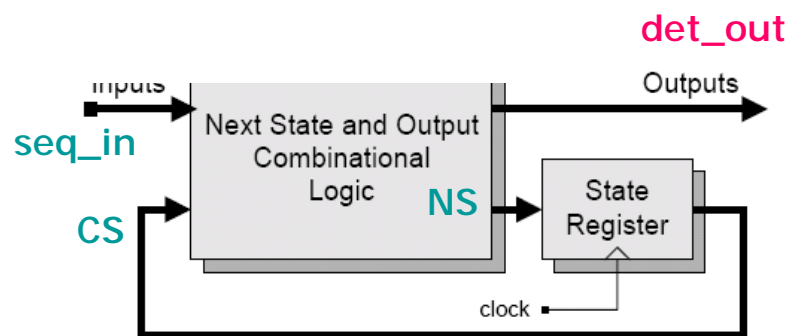
 
# Verilog Code (4/4)

```
// combinational part of the Mealy FSM
// determine the detection output
always @(CS, seq_in) begin
    #2
    case (CS)
        s0: det_out = 0;
        s1: det_out = 0;
        s2: det_out = 0;
        s3: det_out = (seq_in==1) ? 1 : 0;
        default: det_out = 0;
    endcase
end
endmodule
```



9


## Simulation Result

 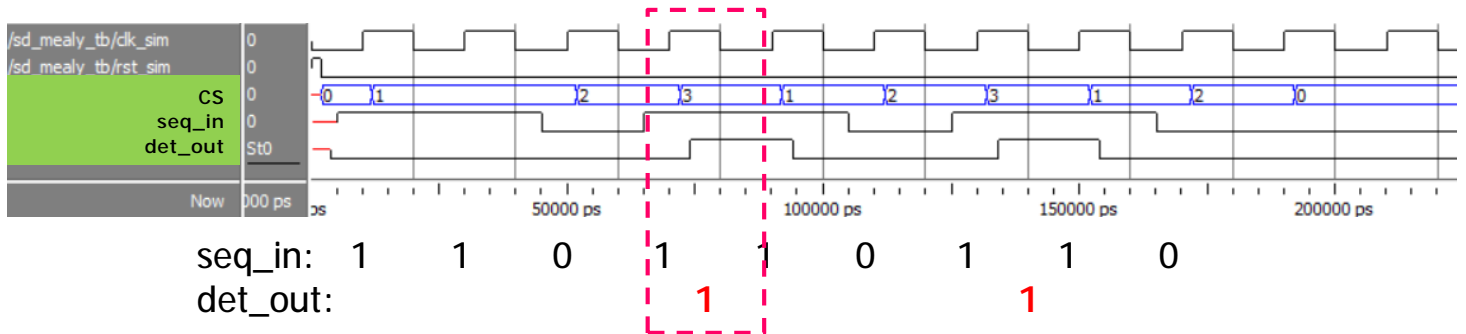

進入state S3時，此時seq\_in為1  
因此det\_out立即變為1，與clk不同步

10



# Design 2: Moore Machine

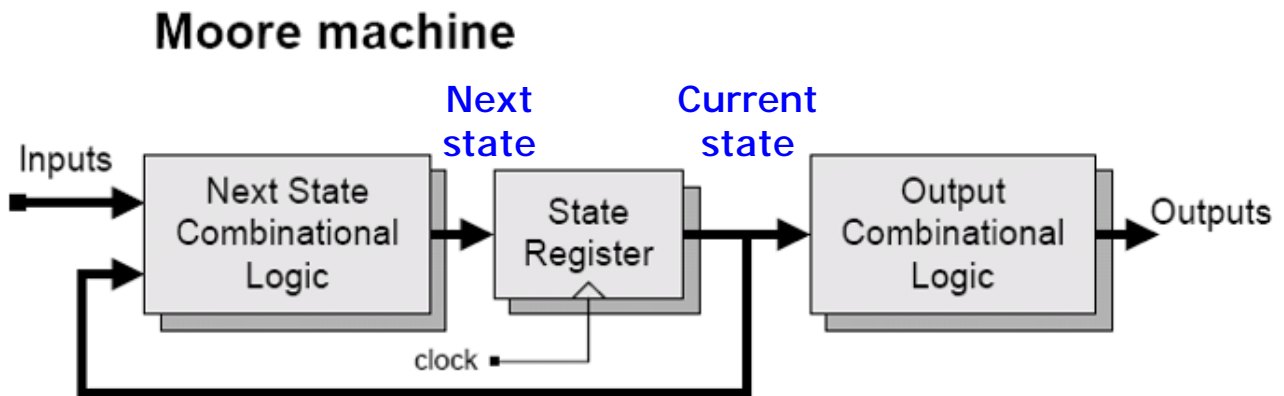

11

## Moore Machine State Diagram

n Target sequence: **1011**

  

12

# Verilog Code (1/4)


```

module sd_moore(clk, rst, seq_in, det_out, state_out);
    input clk, rst, seq_in;
    output reg det_out;
    output [2:0] state_out;

    parameter
        s0=3'b000, // no valid bit
        s1=3'b001, // valid seq: 1
        s2=3'b010, // valid seq: 10
        s3=3'b011, // valid seq: 101
        s4=3'b100; // valid seq: 1011

```

Five states

 

13

# Verilog Code (2/4)


```

reg [2:0] CS, NS;
// CS: current state
// NS: next state


assign state_out = CS;

// sequential part of the Moore FSM
always @(posedge clk, posedge rst) begin
    #2
    if (rst==1)
        CS = s0;
    else
        CS = NS;
end

```

 



Moore machine

 

14
  
## Verilog Code (3/4)



```
// combinational part of the Moore FSM
// determine the next state
always @(CS, seq_in) begin
    #2
    case (CS)
        s0: NS = (seq_in==1) ? s1 : s0;
        s1: NS = (seq_in==1) ? s1 : s2;
        s2: NS = (seq_in==1) ? s3 : s0;
        s3: NS = (seq_in==1) ? s4 : s2;
        s4: NS = (seq_in==1) ? s1 : s2;
        default: NS = s0;
    endcase
end
```



15
  
## Verilog Code (4/4)



```
// combinational part of the Moore FSM
// determine the detection output
always @(CS) begin
    #2
    case (CS)
        s0: det_out = 0;
        s1: det_out = 0;
        s2: det_out = 0;
        s3: det_out = 0;
        s4: det_out = 1;
        default: det_out = 0;
    endcase
end
endmodule
```



16



# Simulation Result

 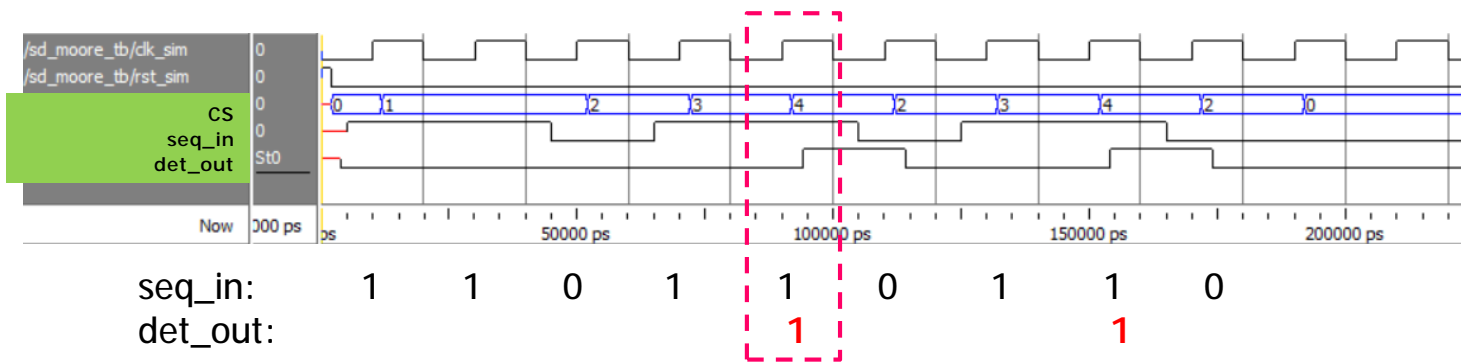

進入state S4時，`det_out`變為1，與clk同步

17

## 作業描述

- n 請利用Mealy及Moore兩種FSM，設計兩個sequence detector電路
- n Target sequence: **10111**
- n Input sequence: **11101111011101110111000**
- n Detection output: **00000010000100010001000**

18

## 作業繳交

---

- n 繳交之作業檔案請以”您的學號\_04”(ex. **S0754000\_04**)命名，包含
  - l Verilog原始檔 (請全部壓縮成一個**S0754000\_04.zip**)
  - l 作業報告檔 (請參考範本 **S0754000\_04.ppt**)
- n 繳交方式：彰化師大雲端學院，課程作業區，以附檔作答
- n 繳交期限：**2019/12/25 (三) 12:00**
- n 有關課程及作業相關問題，可於FB社團 (**2019\_硬體描述語言**) 提出討論